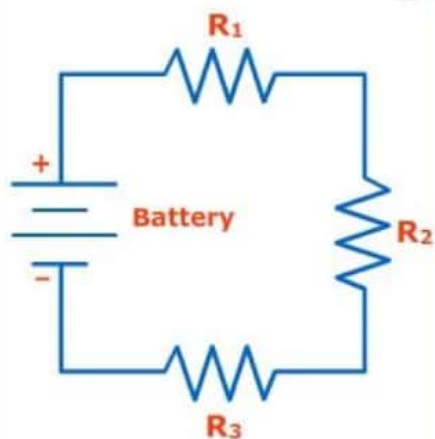


# RESISTANCE

## 1 Resistance



The opposing effect to the flow of current is known as Resistance of the conductor. It is denoted by "R".

$$R = \frac{\rho l}{A}$$

$\rho$  = Resistivity


$l$  = Length

A = Area

Resistance (R) is measured in **Ohm** ( $\Omega$ ).

## 2 Combination

### i Series

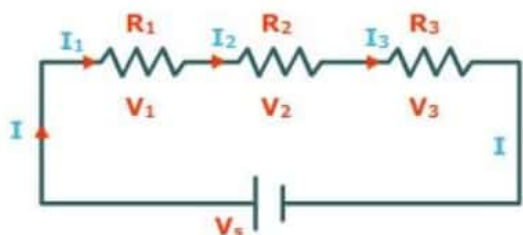

- The current passing through the individual resistance is same and its equal to magnitude of current that comes from the battery.

$$I = I_1 = I_2 = I_3$$


- The sum of the voltage across the individual resistance is equal to the voltage of the battery.

$$V = V_1 + V_2 + V_3$$

- $R_{eq} = R_1 + R_2 + R_3$

- The equivalent resistance of the circuit is always greater than the value of resistance in the circuit.

### ii Parallel

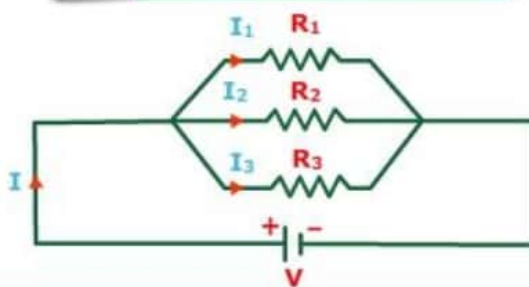

- The sum of current passing through each resistance is equal to the total current coming from the battery.

$$I = I_1 + I_2 + I_3$$

- The voltage across the individual resistance is same and is equal to the voltage of the battery.


$$V = V_1 = V_2 = V_3$$

- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

- The equivalent resistance of the circuit is always less than the smallest value of resistance in the circuit.

# GROUPING OF CELLS

## 1 CELLS IN SERIES

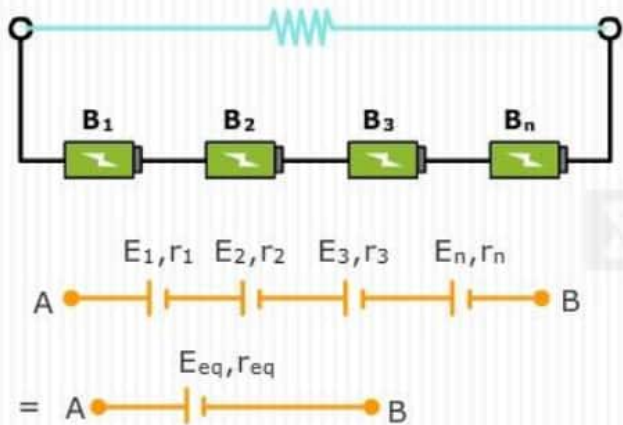

Equivalent EMF

$$E_{eq} = E_1 + E_2 + \dots + E_n$$

Equivalent internal resistance


$$r_{eq} = r_1 + r_2 + r_3 + r_4 + \dots + r_n$$

In  $n$  cells each of emf  $E$  are arranged in series and if  $r$  is internal resistance of each cell, then the total emf is equal to  $nE$

and, current in the circuit,

$$I = \frac{nE}{R + nr}$$

## 2 CELLS IN PARALLEL

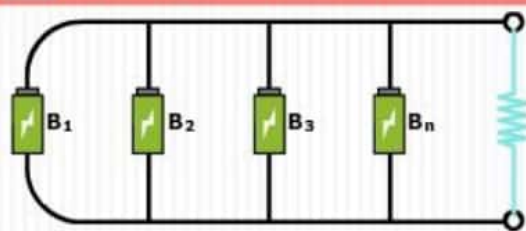

$$E_{eq} = \frac{E_1/r_1 + E_2/r_2 + \dots + E_n/r_n}{1/r_1 + 1/r_2 + \dots + 1/r_n}$$


$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$

If  $m$  cells, each of emf  $E$  and internal resistance  $r$  be connected in parallel and if this combination is connected to an external resistance ( $R$ ) then the emf of the circuit =  $E$ .

internal resistance of the circuit =  $\frac{r}{m}$

and 
$$I = \frac{E}{R + \frac{r}{m}} = \frac{mE}{mR + r}$$

## 3 CELLS IN MULTIPLE ARC

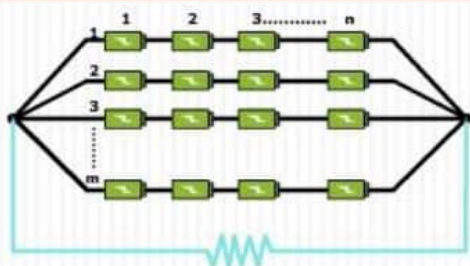

$n$  = number of rows

$m$  = number of cells in each row

Current 
$$I = \frac{mE}{R + \frac{mr}{n}}$$

for maximum current  $nR = mr$

## 4 ELECTRICAL POWER

$$\text{Power, } P = \frac{V \cdot dq}{dt} = VI = I^2 R = \frac{V^2}{R}$$

$$\text{Work, } W = VIt = I^2 Rt = \frac{V^2}{R} t$$


$$\text{Heat, } H = I^2 Rt \text{ Joule} = \frac{I^2 Rt}{4.2} \text{ calorie}$$



# CELLS AND ELECTRIC POWER

## COMBINATIONS OF CELLS

### 1 CELL IN SERIES

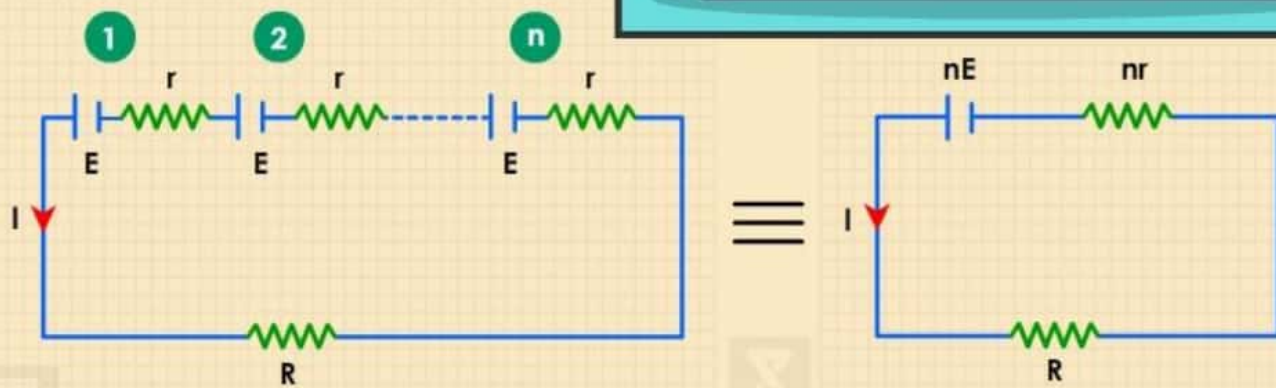


- Net EMF of the cells =  $nE$ ,
- Total internal resistance =  $nr$ ,
- Hence total resistance of the circuit =  $nr + R$ ,

$$I = \frac{\text{net EMF}}{\text{Total Resistance}} = \frac{nE}{nr + R}$$

**Case I** If  $nr \ll R$ , then  $I \cong nE/R$  i.e. current obtained from the cells is approximately equal to **n times** the current obtained from a single cell.

**Case II** If  $nr \gg R$ , then  $I \cong nE/nr = E/r$  i.e. current obtained from the combination of **n cells** is nearly **the same** as obtained from a single cell.

### 2 CELL IN PARALLEL

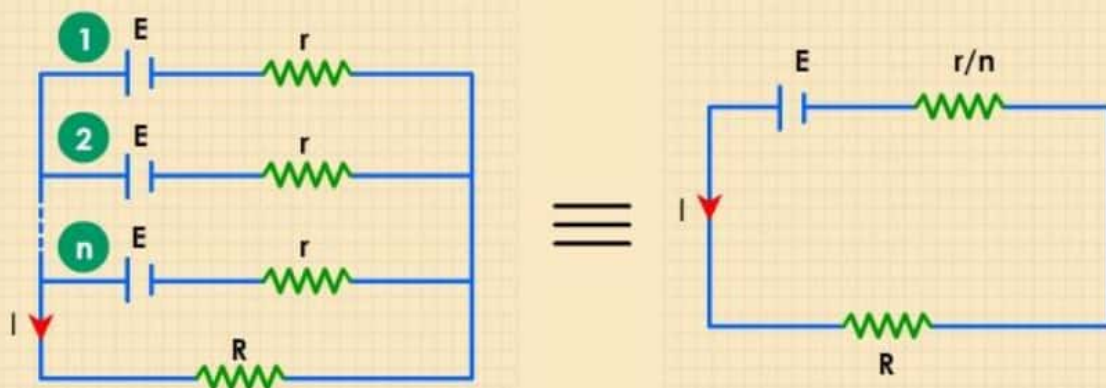

### When E.M.F's and internal resistance of all the cells are equal


- E.M.F of battery =  $E$ .
- Total internal resistance of the combination of  $n$  cells =  $r/n$
- Total resistance of the circuit =  $(r/n) + R$

$$I = \frac{\text{net E.M.F}}{\text{Total Resistance}} = \frac{E}{(r/n)+R} = \frac{nE}{r+nR}$$

**Case I** If  $r \ll R$ , the  $I \cong nE/nR = E/R$ ; then total current obtained from combination is approximately equal to current given by one cells only.


**Case II** If  $r \gg R$ , then  $I \cong nE/r$ ; then total current is approximately equal to  $n$  times the current given by one cell.
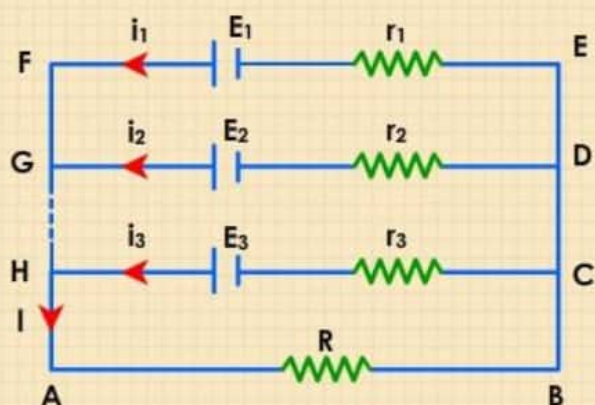
### When E.M.F's and internal resistance of all the cells connected in parallel are different



$$I = \frac{\sum_{i=0}^n \frac{E_i}{r_i}}{1+R \sum \frac{1}{r_i}} \quad \text{and} \quad E_{\text{eq.}} = \frac{\sum \frac{E_i}{r_i}}{\sum \frac{1}{r_i}}, \quad r_{\text{eq.}} = \frac{1}{\sum \frac{1}{r_i}}$$

### 3 CELL IN MIXED GROUPING

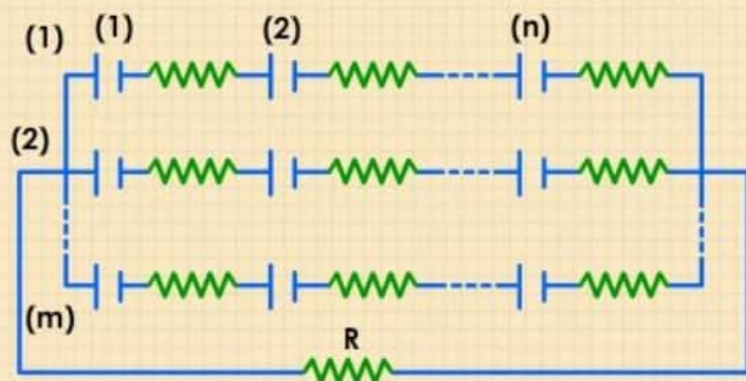

$$\text{Total resistance of the circuit} = \left[ \left( \frac{nr}{m} \right) + R \right]$$

$$I = \frac{\text{net E.M.F}}{\text{Total Resistance}} = \frac{nE}{(nr/m)+R} = \frac{nmE}{nr+mR}$$

## ELECTRICAL POWER

The energy liberated per second in a device is called its power. The electrical power  $P$  delivered by an electrical device is given by

$$P = \frac{dq}{dt} V$$

$$P = VI$$

$$P = I^2R$$

$$P = \frac{V^2}{R} \quad \text{watt}$$

# INSTRUMENTS MEASURING VARIOUS ELECTRICAL QUANTITIES


## 01 AMMETER

A shunt (small resistance) is connected in parallel with galvanometer to convert it into ammeter.

$I_G$  = Current through galvanometer

$R_G$  = Resistance of galvanometer


$$S = \frac{I_G R_G}{I - I_G}$$

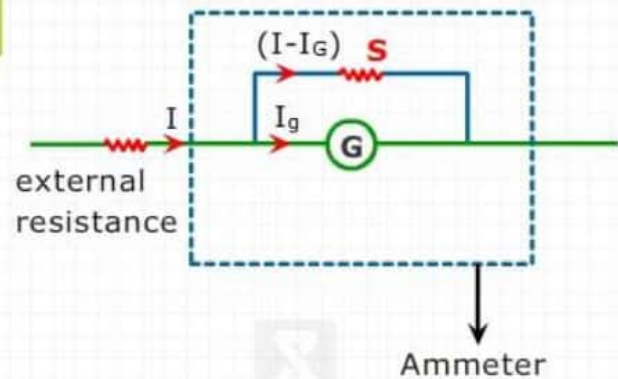

## 02 VOLTMETER

A high resistance is put in series with galvanometer. It is used to measure potential difference across a resistor in a circuit.

$$I_G = \frac{V}{R_G + R}$$

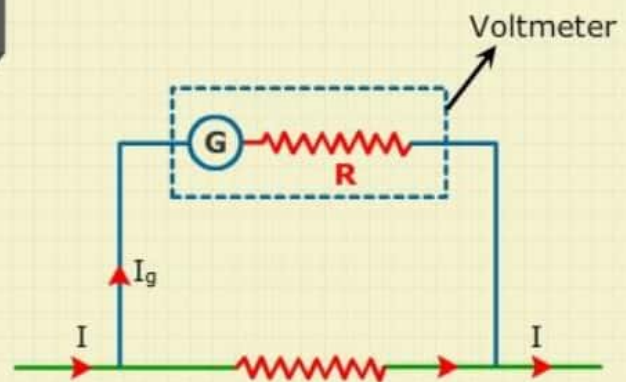


## 03 METRE-BRIDGE

$$S = \frac{R(100 - l)}{l}$$

$R$  = Resistance taken in the resistance box

$l$  = Length measured

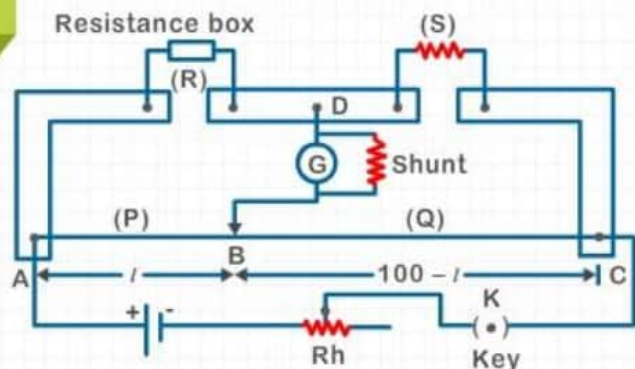

# POTENTIOMETER

$l$  = Length


$A$  = Area of cross-section

$\rho$  = Resistivity of material

$I$  = Current

$$V = I\rho \frac{l}{A}$$

Part II

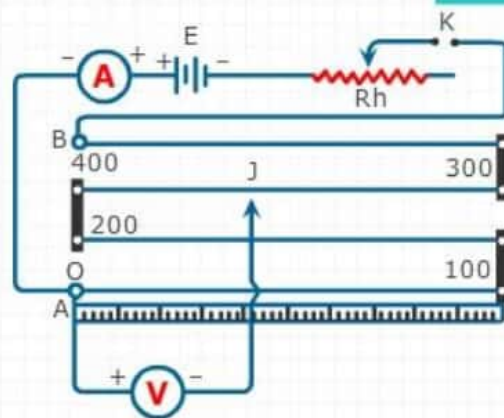

## APPLICATION OF POTENTIOMETER


### APPLICATION-01

To find EMF of an unknown cell and compare EMF of two cells

$l_1$  = Balancing length when key is between gaps of terminal 1 and 2

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

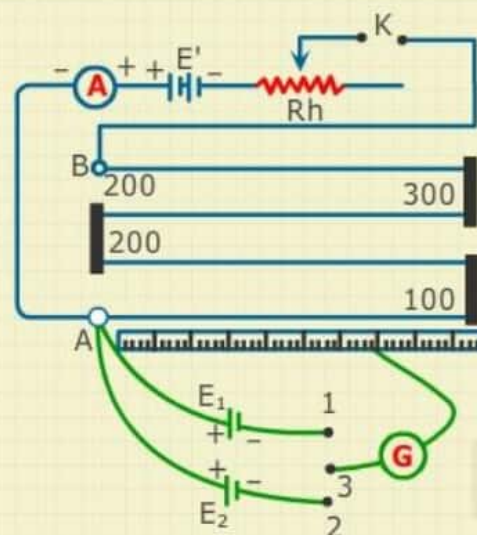
$l_2$  = Balancing length when key is between gaps of terminal 2 and 3


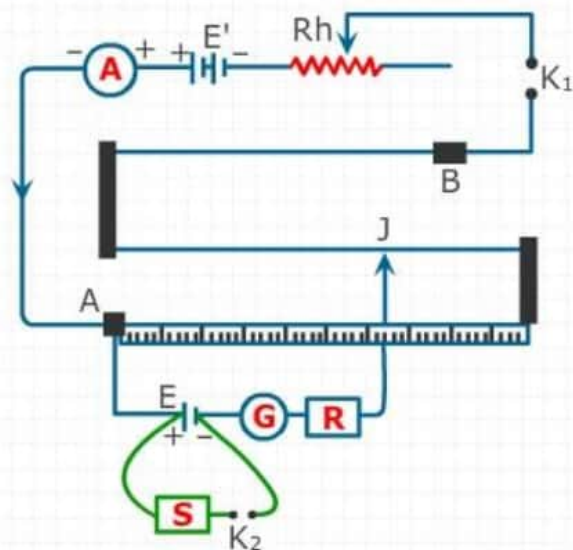
### APPLICATION-02

To find the internal resistance of a cell

$$r' = \left[ \frac{l_1 - l_2}{l_2} \right]$$



### APPLICATION-03

To find current if resistance is known

$$I = \frac{Xl_1}{R_1}$$